




Losses in converters

Thursday, March 18, 2021 9:24 AM

→ There are no ideal elements.


→ Let us model a practical inductor.

It only includes copper loss

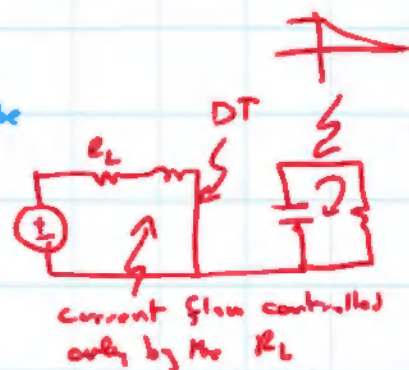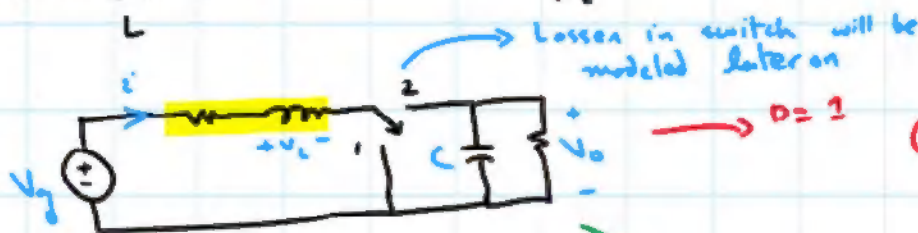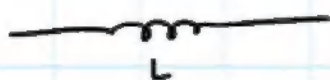

$$V_L(t) = V_g - i(t)R_L$$

$$i_c(t) = \frac{-v(t)}{R}$$

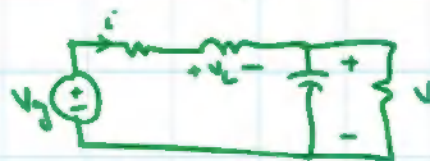

$$V_L(t) = V_g - i(t)R_L - v(t)$$

$$i_c(t) = i(t) - \frac{v(t)}{R}$$

Apply the SRA.

$$V_L(t) = V_g - IR_L$$

$$i_c(t) = -\frac{V}{R}$$

$$V_L(t) = V_g - IR_L - V$$

$$i_c(t) = I - \frac{V}{R}$$

Volt-sec balance through $V_L(t)$ waveform

$$\langle V_L(t) \rangle = DT_s(V_g - IR_L) + D'T_s(V_g - IR_L - V) = 0$$

For steady state it is zero


$$0 = \underbrace{V_g}_{\text{g/p}} - \underbrace{IR_L}_{\text{unknown}} - \underbrace{D'V}_{\text{o/p}} \quad \text{--- (A)}$$

To solve (A) capacitor charge-sec balance is used

$$\langle i_c(t) \rangle = DT_s(-V/R) + D'T_s(I - V/R) = 0$$

$$0 = D'I - V/R \quad \text{--- (B)}$$

using (A) & (B)

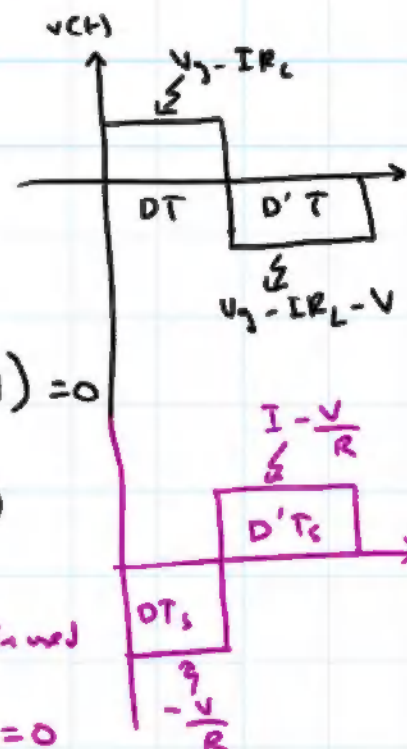

(C)


using (A) & (B)

$$m(D) = \frac{V}{V_g} = \frac{1}{D'} \left[\frac{1}{1 + \frac{R_L}{D'^2 R}} \right] \quad \text{--- (C)}$$

plot $m(D)$ as a function of D and R_L/R

E_V C

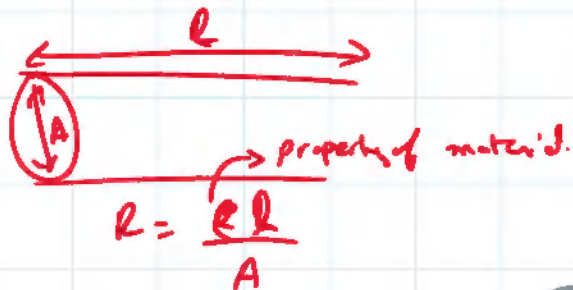- if $R_L = 0$ then $V/V_g = \frac{1}{D'} = \frac{1}{1-D}$ and it shows ideal Buck converter
- if $R_L \ll D'^2 R$ then $\frac{V}{V_g} \approx \frac{1}{D'}$
- if $R_L > D'^2 R$ then $\frac{V}{V_g}$ is reduced
- At $D=1$ the $m(D)$ tends to zero.




$A \uparrow$ winding space occupy \uparrow
 larger core \uparrow power density \downarrow

Let us derive (C) using DC Transformer

we need (A) and (B)

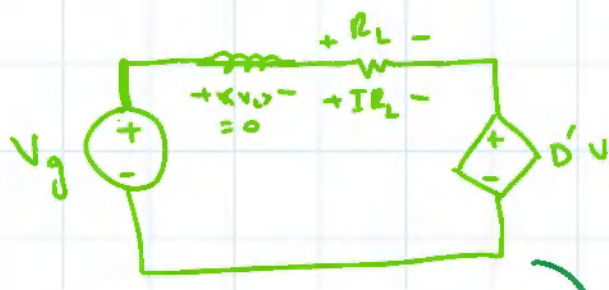
(A) $\rightarrow V_g - I R_L - D' V = 0 = \langle v_L \rangle$


- V_g : i/p voltage, Independent voltage source
- $I R_L$: voltage drop, modeled using R_L
- $D' V$: o/p voltage, Controlling parameter, modeled as a dependent source.



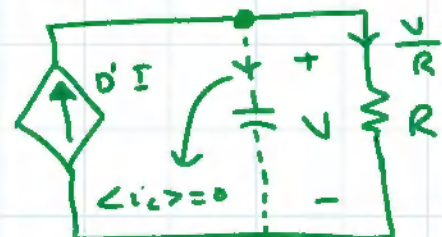(B) $\rightarrow D' I - \frac{V}{R} = 0 = \langle i_C \rangle$


- $D' I$: controlled variable current, Dependent source
- $\frac{V}{R}$: capacitor current = 0



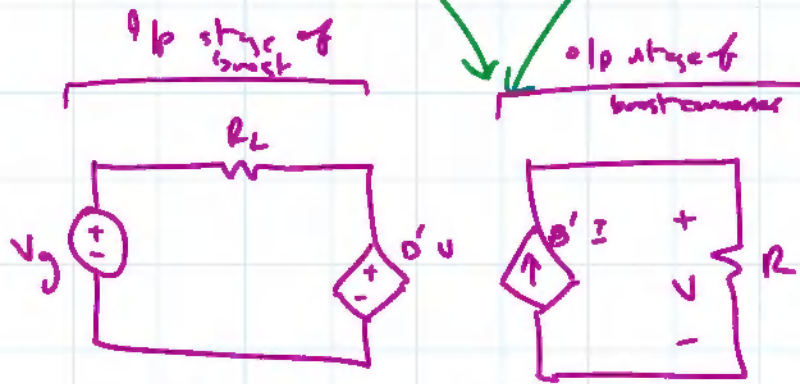

$$1: D'(10)$$

$$m(1): 1$$

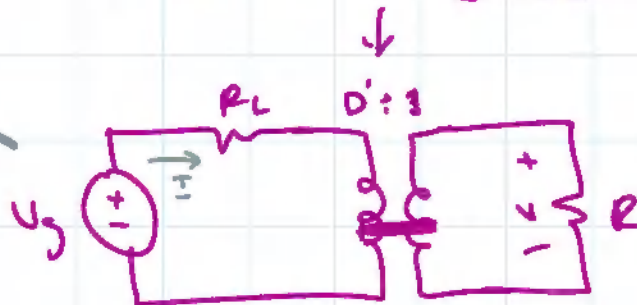

$$\frac{N_p}{N_s} = \frac{V_p}{V_s}$$

$$D': 1 = \frac{V_p}{V_s}$$

$$V_s = \frac{V_p}{D'}$$

$\eta = ?$

$$P_{in} = V_g I$$

$$P_o = V D' I$$

$$\eta = \frac{V D' I}{V_g I}$$


$$= \frac{V}{V_g} D'$$

putting value of V

Transfer primary side to the sec side.

$$V_g \xrightarrow{\text{sec}} \frac{V_g}{D'}$$
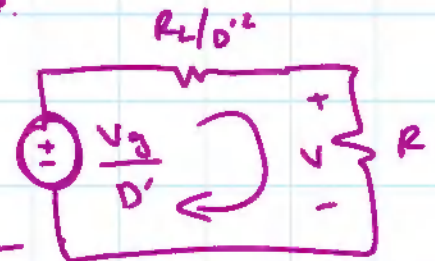
$$R_L \xrightarrow{\text{sec}} R_L / D'^2$$



$$V = \frac{V_g}{D'} \left(\frac{R}{R + \frac{R_L}{D'^2}} \right) \quad \left. \vphantom{\frac{V_g}{D'}} \right\} V_{DR}$$

$$\eta = \frac{1}{1 + \frac{R_L}{D'^2 R}}$$

Matlab plotting

$$\frac{V}{V_g} = \frac{1}{D'} \frac{1}{1 + \frac{R_L}{D'^2 R}}$$

(D)

Ey (C) and (D) are same.

plot eq (C) & (E) in matlab with addition to different ratio of $\frac{R_L}{R}$ given in the book